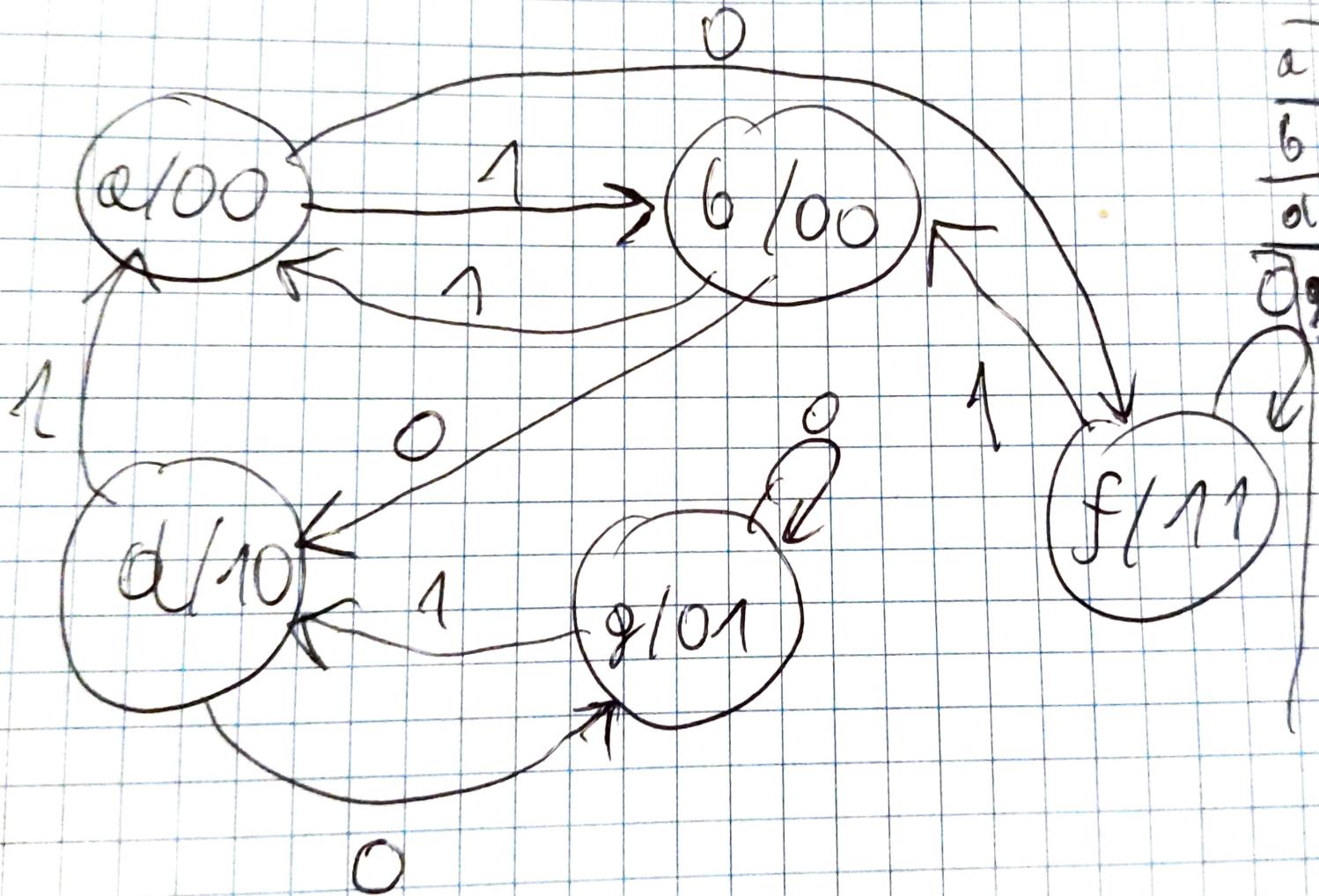


②

Zminimalizowany układ:



q	q ₀	q ₁	q ₂	q ₃	q ₄
z	x	x	x	x	x
a	f	b	0	0	0
b	a	*	0	0	0
d	g	a	1	0	0
e	g	d	0	1	1
f	f	b	1	1	1